



## General terms

### Electrical power $P$

$$P = \frac{V^2}{R} = I^2 R \text{ [W]}$$

### Current density $J$

$$J = \frac{I}{A} \text{ [A/m}^2\text{]}$$

### Resistance $R$

$$R = \frac{V}{I} \text{ [\Omega]} \quad (\text{Ohm's law})$$

### Conductance $G$

$$G = 1/R \text{ [2S]}$$

### Quantity of electricity, charge $Q$

$$q = \int i \cdot dt \text{ [C]}$$

### Capacitance $C$

$$C = \frac{Q}{V}$$


### Inductance $L$

$$L = N \frac{\phi}{I} = N \frac{\phi_L}{i}$$

## Series Connection

**Total resistance**  $R_s$  (according to s 26)


$$R_s = R_1 + R_2 + R_3 + \dots$$

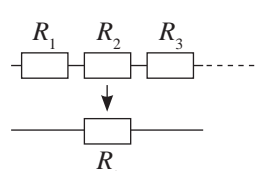
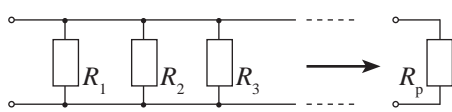
## Parallel Connection

**Total resistance**  $R_p$  (according to s 30)

$$\frac{1}{R_p} = \frac{1}{R_1} + \frac{1}{R_2} + \frac{1}{R_3} + \dots$$



## Inductance

### Inductance in series

$$L = L_1 + L_2 + L_3 + \dots$$


### Inductance in parallel

$$\frac{1}{L} = \frac{1}{L_1} + \frac{1}{L_2} + \frac{1}{L_3} + \dots$$

## Electric field
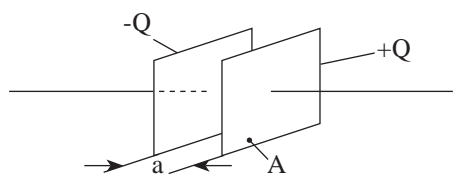
### Capacitance $C$ of a capacitor

$$C = \frac{\epsilon_o \cdot \epsilon_r \cdot A}{a} \text{ [F]}$$



### Capacitors connected in parallel

$$C = C_1 + C_2 + C_3 + \dots$$

### Capacitors connected in series

$$\frac{1}{C} = \frac{1}{C_1} + \frac{1}{C_2} + \frac{1}{C_3} + \dots$$

## Transfer function

### Series combination

$$u^{(s)} \rightarrow \boxed{F_1(s)} \rightarrow \boxed{F_2(s)} \rightarrow v^{(s)} \quad F(s) = F_1(s) \cdot F_2(s)$$

### Parallel combination

$$u^{(s)} \rightarrow \left[ \begin{array}{c} \boxed{F_1(s)} \\ \boxed{F_2(s)} \end{array} \right] \rightarrow v^{(s)} \quad F(s) = F_1(s) + F_2(s)$$

### Feedback rule

$$u^{(s)} \rightarrow \left[ \begin{array}{c} \boxed{F_1(s)} \\ \boxed{F_2(s)} \end{array} \right] \rightarrow v^{(s)} \quad F(s) = \frac{F_1(s)}{1 + F_1(s) \cdot F_2(s)}$$